



## EE 4550L IC Hardware Security and Trust


### Lab 1 – Test 4-bit adder/subtractor in Xilinx Vivado

(Note: Write your TA's name and your login on the report)

#### Objective


The objective of this lab is to practice writing VHDL code and testbench. Xilinx Vivado is used to simulate VHDL code and testbench.

#### A. 4-bit Binary Ripple Carry Adder

 

1. Create truth table for 1-bit full adder.
2. Create basic logic gates in VHDL code for 1-bit full adder.
3. Create 1-bit full adder in VHDL code.
4. Simulate testbench and 1-bit full adder in Vivado. Verify the simulation waveform with truth table.
5. Create 4-bit binary ripple carry adder in VHDL code.
6. Create a testbench for 4-bit binary ripple carry adder with the following testing cases.  
case 1: C0=0, A=0110, B=0011 case 2: C0=0, A=1010, B=0011  
case 3: C0=1, A=0100, B=0101 case 4: C0=1, A=0101, B=0110
7. Simulate testbench and circuit 4-bit binary adder in Vivado.

#### B. 4-bit Binary Adder/Subtractor

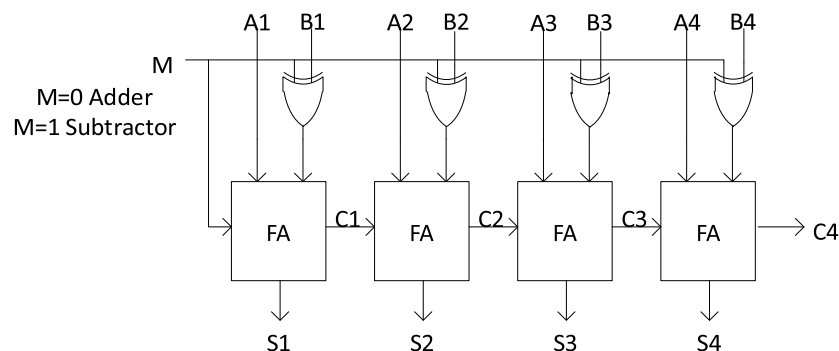

1. Create 4-bit binary adder/subtractor in VHDL code.
2. Create a testbench for 4-bit binary adder/subtractor with the following testing cases.  
case 1: M=0, A=0110, B=0011 case 2: M=0, A=1010, B=0011  
case 3: M=1, A=0100, B=0101 case 4: M=1, A=0101, B=0110
3. Simulate testbench and circuit 4-bit binary adder/subtractor in Vivado.

### **Lab Report (30 points)**

A LAB REPORT SHOULD BE SUBMITTED INDIVIDUALLY. This should include:

Truth table of 1-bit full adder.

All related VHDL code (including testbench).

Simulation waveform of 1-bit full adder, 4-bit adder, and 4-bit adder/subtractor. Label binary value of waveforms.

Question: How many input patterns are required for exhaustive testing on 4-bit adder and adder/subtractor? Why?

## Appendix

Xilinx Vivado tutorial:


Start Xilinx Vivado by typing “vivado &” in terminal. Click “Create New Project”.




Click “Next”.



 Type “Project name”, select “Project location”, hit “Next”.



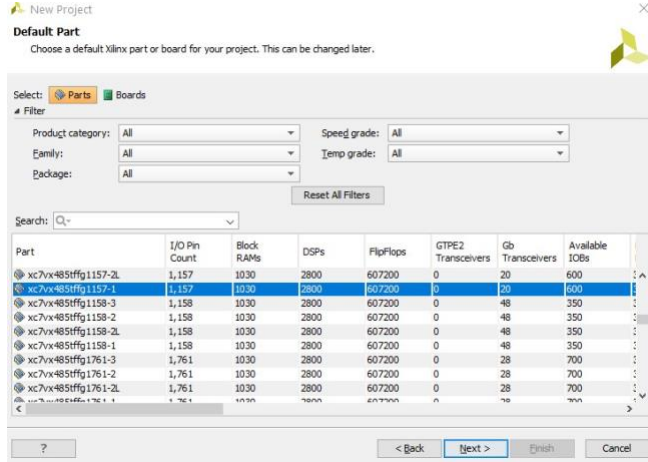
Click “Next” until the following window, select “xc7vx485tffg1157-1”, click “Next”.




Click “Finish”.



Click “Add Sources” in Project Manager.

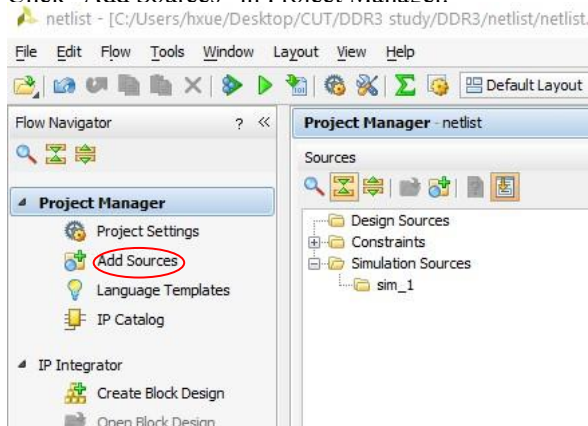

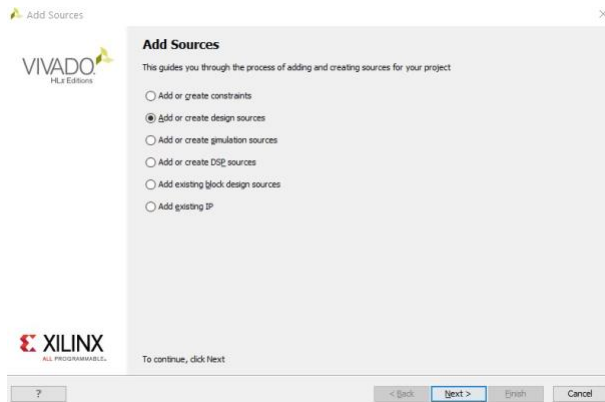Select “Add or create design sources”, click “Next”, add or create RTL code and testbench.



Click “Run Simulation” in Simulation.

```
-- 2 inputs AND gate library
IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity AND2 is
    Port ( A : in  STD_LOGIC; -- AND gate input
          B      : in  STD_LOGIC; -- AND gate input
          C : out STD_LOGIC); -- AND gate output end
AND2;

architecture Behavioral of AND2 is begin
    C      <= A and B; -- 2 input AND gate end
Behavioral;
```

```
-- Testbench for AND gate
library IEEE;
use
IEEE.STD_LOGIC_1164.ALL;
entity AND2TestBench is end
AND2TestBench;

architecture Behavioral of AND2TestBench is
component AND2 is
    Port (A,B:in std_logic;
          C: out std_logic );
end component; --inputs
signal a: std_logic:= '0';
signal b: std_logic:= '0';
--outputs
signal c : std_logic;
constant period : time := 1ns;

begin
    uut: AND2 PORT MAP (a=>A,b=>B,c=>C);
    a<=not a after period; b<=not b
    after period*2;

end Behavioral;
```